

1) Consider the following number in binary. Calculate the decimal number based on the given formats:

$$(1010011)_2 = (?)_{10}$$

- a. Sign-Magnitude
- b. Unsigned
- c. 1's Complement
- d. 2's Complement


2) Consider the following Boolean expression:

$$F = \overline{\overline{a} + d} \cdot \overline{b + \overline{c}} \cdot \overline{\overline{c} + d}$$

- a. Simplify the expression.
- b. Construct a gate level of the simplified function.
- c. Construct a gate level of the same function only using NAND gates.

3) The state diagram of a Finite State Machine (FSM) is given below:

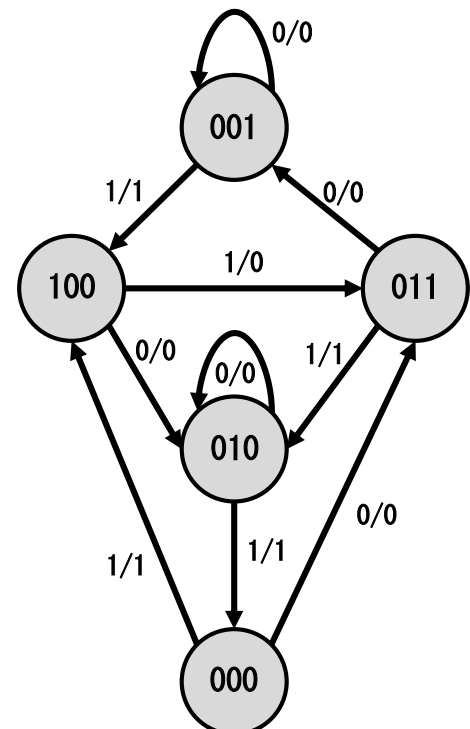- a. Determine this machine's type. (Whether the following machine is a Mealy State Machine or Moor State Machine)
- b. Based on your answer in the previous section, convert the machine to other type.
- c. Construct the state transition table for the original machine.



**4)** Design a circuit that computes the cube of the input (2 bits), using the minimum size possible ROM.

**5)** Design a circuit with the following conditions:

- Input: 4-bit number A ( $A_3A_2A_1A_0$ )
- Output: Output goes HIGH if A is a multiplier of 2 or 3.
- Using only 8:1 Multiplexer.

**6 – Bonus point)** Using shift registers, Flip-Flops and logic gates design a circuit that computes the 2's complement of a serial input.

If you have any questions regarding this assignment, feel free to contact us.

**Please submit your homework, simulations and projects in the following format:**

Name\_StudentNumber\_HW0 (BillGates\_12345678\_HW0)

Good Luck!